
```
%Recall ==> var(L,Vgs,Vds,Vsb)
%Givens
clc;
% load 180nmos.mat; load 180pmos.mat;
Iref = 100E-6;
L = 1.2;
qm ID = 20;
vqs o = whatisVGS(nch, 'GM ID', 20, 'L', L);
vds_o = vgs_o;
vgs = whatisVGS(nch, 'GM_ID', 20, 'L', L, 'VDS', vds_o);
vds = vgs;
fprintf('Homework 4 - Problem 1\n');
fprintf('\n');
<u>&______</u>
VoutChange = 0.1;
gm = gm_ID*Iref;
qm qds = whatis(nch, 'GM GDS', 'L', L, 'VGS', vqs, 'VDS', vds);
gds = gm / gm_gds;
ro = 1/qds;
VxChange = VoutChange/(gm*ro);
fprintf('i) Corresponding swing at node X --> VxSwing = %d V\n',
VxChange);
fprintf('\n');
JD = whatis(nch, 'ID W', 'L', L, 'VGS', vqs, 'VDS', vds);
W = Iref/JD;
vbias = vds + whatisVGS(nch, 'GM_ID', 20, 'L', L, 'VDS', vds);
fprintf('ii) Width of the devices --> W = %d m\n', W);
fprintf(' Vbias for the circuit --> Vbias = %d V\n', vbias);
fprintf('\n');
§______
iii
vout = [0:0.025:1.8];
gds3 = gm ./ whatis(nch, 'GM_GDS', 'L', L, 'VGS', vgs, 'VDS', vout/2);
ro3 = 1./qds3;
gm3 = gm;
gmb3 = gm3 / whatis(nch,'GM_GMB' , 'GM_ID', gm_ID, 'VDS', vds,'L', L);
r mirror = ro3.*(1+(qm3+qmb3).*ro3)+ro3;
```

```
figure(1);
plot(vout, ro3, '-k', vout, r_mirror, '-r');
legend('Rout of M3', 'Rout of current mirror');
xlabel('Vout (V)'); ylabel('Resistance (Ohm)');
fprintf('iii) Plots done.');
fprintf('\n');
vov4a = whatis(nch, 'VTH', 'L', L, 'VGS', vgs);
vds4a = 60E-3;
vds4b = 65E-3i
vds4c = 70E-3;
JD4a = whatis(nch, 'ID_W', 'GM_ID', gm_ID', 'L', L, 'VDS', vds4a);
W4a = Iref / JD4a;
JD4b = whatis(nch, 'ID_W', 'GM_ID', gm_ID , 'L', L, 'VDS', vds4b);
W4b = Iref / JD4b;
JD4c = whatis(nch, 'ID_W', 'GM_ID', gm_ID', 'L', L, 'VDS', vds4c);
W4c = Iref / JD4c;
vout4a = 2 * vds4a;
vout4b = 2 * vds4b;
vout4c = 2 * vds4c;
Homework 4 - Problem 1
i) Corresponding swing at node X --> VxSwing = 7.495329e-04 V
ii) Width of the devices --> W = 2.222647e-04 m
    Vbias for the circuit --> Vbias = 9.102323e-01 V
iii) Plots done.
```

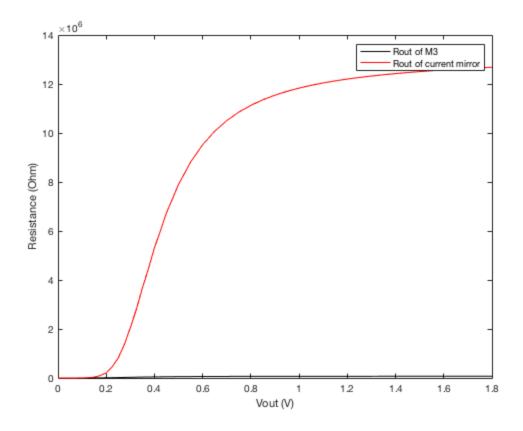

Published with MATLAB® R2018b