

Figure 1: NMOS schematic

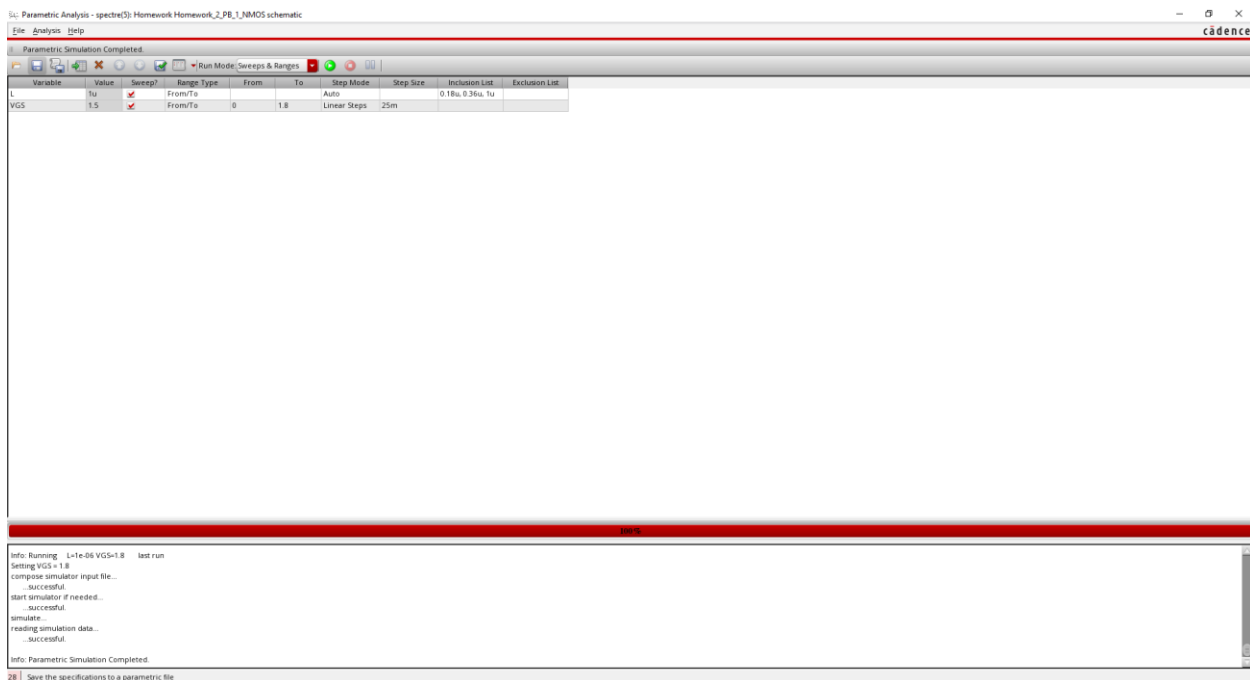


Figure 2: NMOS simulation window

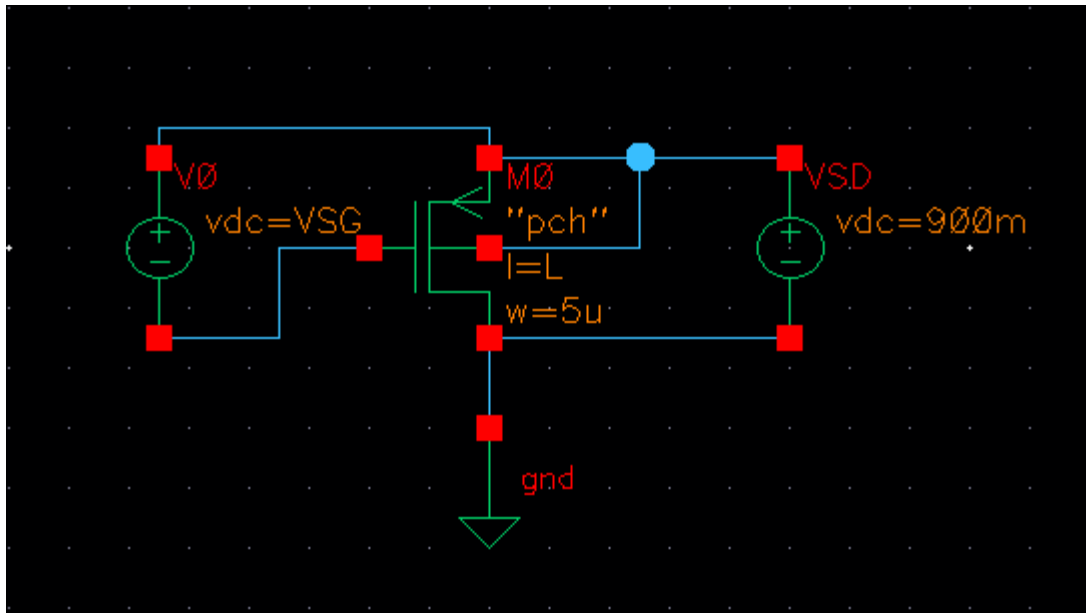


Figure 3: PMOS schematic

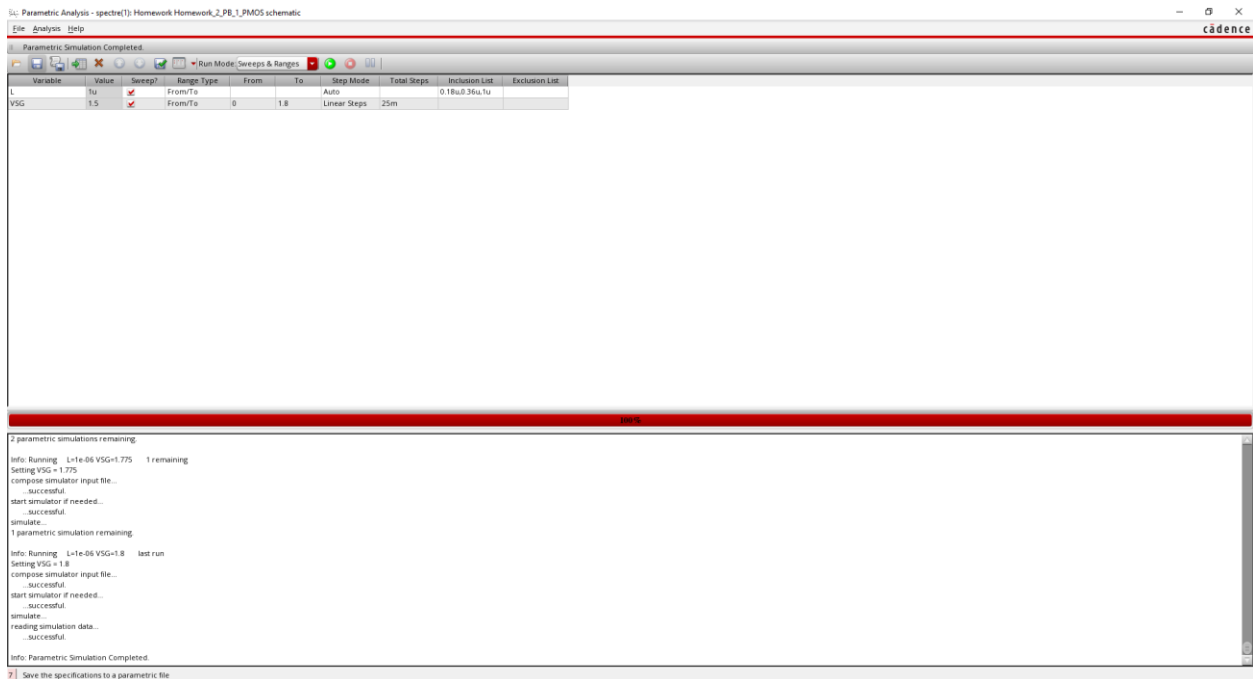


Figure 4: PMOS simulation window

```

Id_over_W_18P = readData{1,28}(:,1);
Id_over_W_36P = readData{1,29}(:,1);
Id_over_W_1P = readData{1,30}(:,1);

%Plot Data
%gm/Id vs Vov
figure(1)
hold on;
plot(Vov_18N, gm_over_Id_18N, 'k-');
plot(Vov_36N, gm_over_Id_36N, 'k--');
plot(Vov_1N, gm_over_Id_1N, 'k:');
plot(Vov_18P, gm_over_Id_18P, 'ko');
plot(Vov_36P, gm_over_Id_36P, 'kx');
plot(Vov_1P, gm_over_Id_1P, 'k^');
legend('NMOS L = 180nm', 'NMOS L = 360nm', 'NMOS L = 1um', 'PMOS L = 180nm', 'PMOS L = 360nm', 'PMOS L = 1um', 'Location', 'east', 'NumColumns', 2);
title('Plot of g_m/I_D vs V_O_V for different channel lengths and types');
xlabel('V_O_V (V)');
ylabel('g_m/I_D (S/A)');
grid on;
grid minor;

%gm/gds vs gm/Id
figure(2)
hold on;
plot(gm_over_Id_18N, gm_over_gds_18N, 'k-');
plot(gm_over_Id_36N, gm_over_gds_36N, 'k--');
plot(gm_over_Id_1N, gm_over_gds_1N, 'k:');
plot(gm_over_Id_18P, gm_over_gds_18P, 'ko');
plot(gm_over_Id_36P, gm_over_gds_36P, 'kx');
plot(gm_over_Id_1P, gm_over_gds_1P, 'k^');
legend('NMOS L = 180nm', 'NMOS L = 360nm', 'NMOS L = 1um', 'PMOS L = 180nm', 'PMOS L = 360nm', 'PMOS L = 1um', 'Location', 'southeast', 'NumColumns', 2);
title('Plot of g_m/g_ds vs g_m/I_D for different channel lengths and types');
xlabel('g_m/I_D (S/A)');
ylabel('g_m/g_ds (unitless)');
grid on;
grid minor;

%ft vs gm/Id
figure(3)
hold on;
plot(gm_over_Id_18N, ft_18N, 'k-');
plot(gm_over_Id_36N, ft_36N, 'k--');
plot(gm_over_Id_1N, ft_1N, 'k:');
plot(gm_over_Id_18P, ft_18P, 'ko');
plot(gm_over_Id_36P, ft_36P, 'kx');
plot(gm_over_Id_1P, ft_1P, 'k^');



```



```

legend('NMOS L = 180nm','NMOS L = 360nm','NMOS L =
    1um','PMOS L = 180nm','PMOS L = 360nm','PMOS L =
    1um','Location','northeast','NumColumns',2);
title('Plot of f_T vs g_m/I_D for different channel lengths and
    types');
xlabel('g_m/I_D (S/A)');
ylabel('f_T (Hz)');
grid on;
grid minor;

%Id/W vs gm/Id
figure(4)
hold on;
plot(gm_over_Id_18N, Id_over_W_18N, 'k-');
plot(gm_over_Id_36N, Id_over_W_36N, 'k--');
plot(gm_over_Id_1N, Id_over_W_1N, 'k:');
plot(gm_over_Id_18P, Id_over_W_18P, 'ko');
plot(gm_over_Id_36P, Id_over_W_36P, 'kx');
plot(gm_over_Id_1P, Id_over_W_1P, 'k^');
legend('NMOS L = 180nm','NMOS L = 360nm','NMOS L =
    1um','PMOS L = 180nm','PMOS L = 360nm','PMOS L =
    1um','Location','northeast','NumColumns',2);
title('Plot of I_D/W vs g_m/I_D for different channel lengths and
    types');
xlabel('g_m/I_D (S/A)');
ylabel('I_D/W (A/m)');
grid on;
grid minor;

```

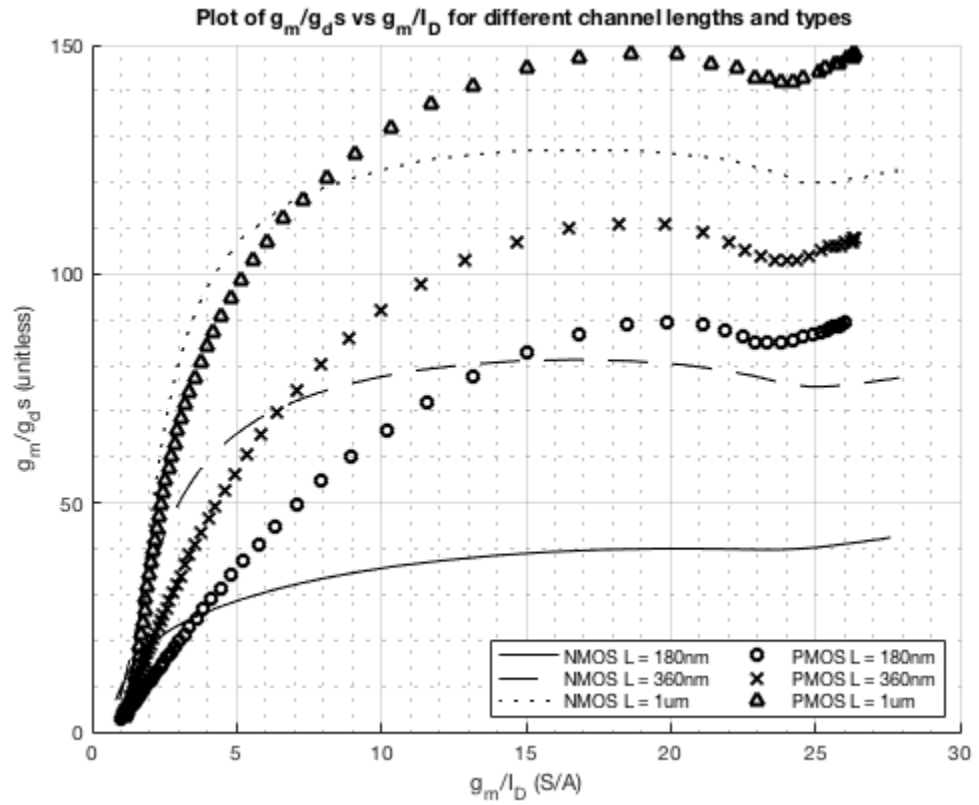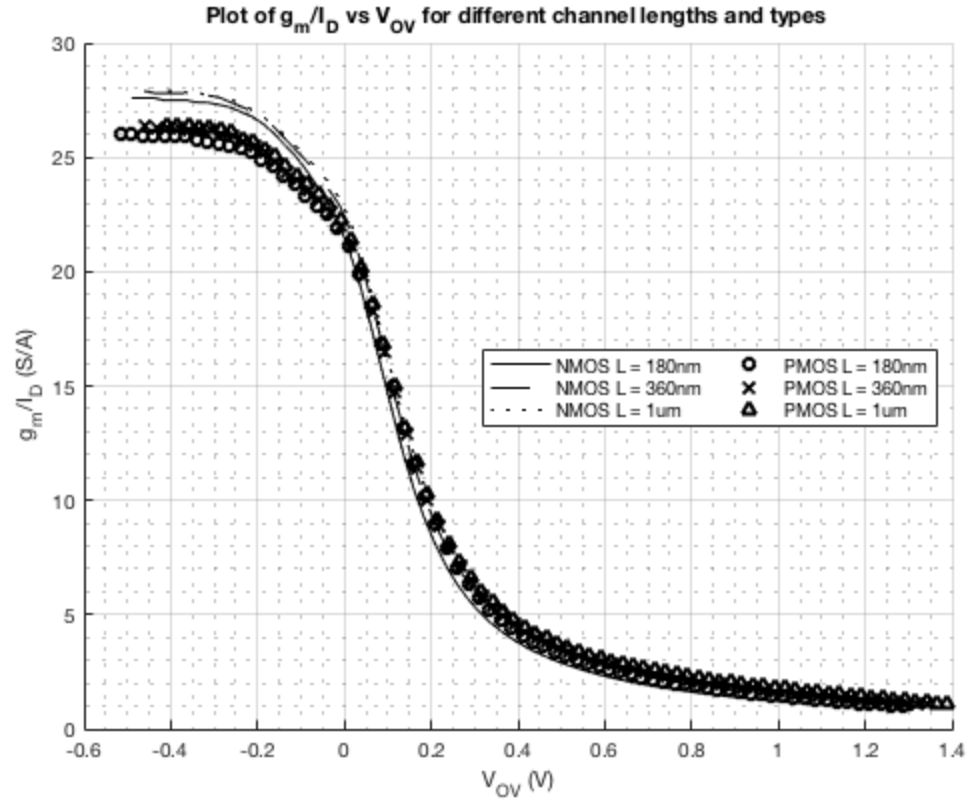

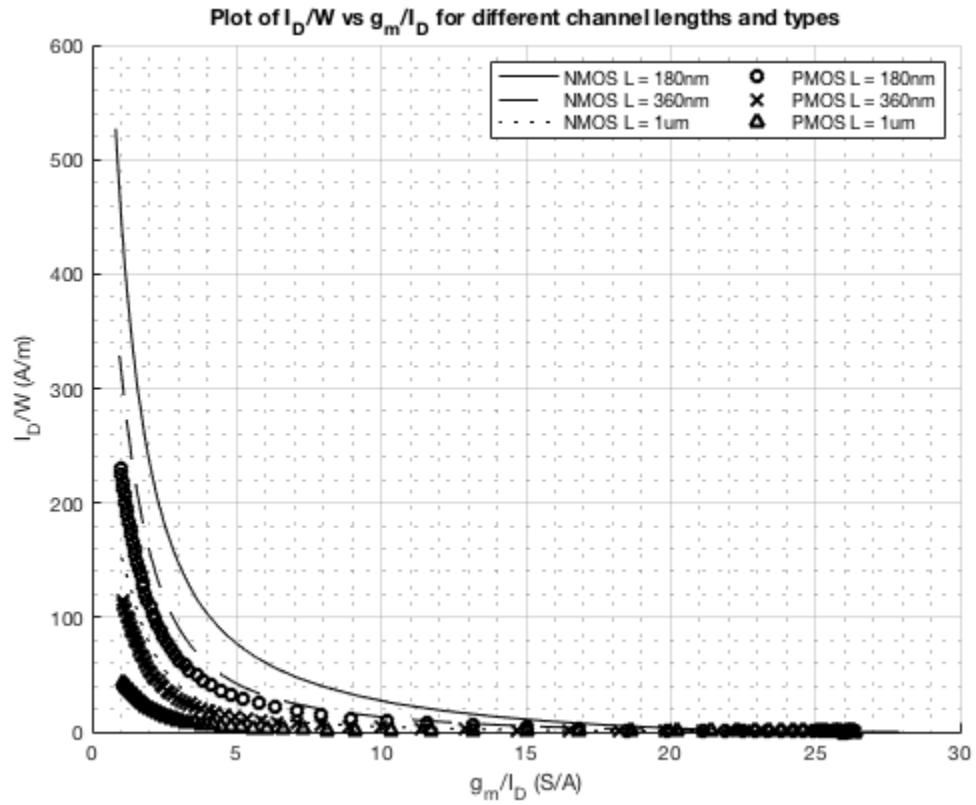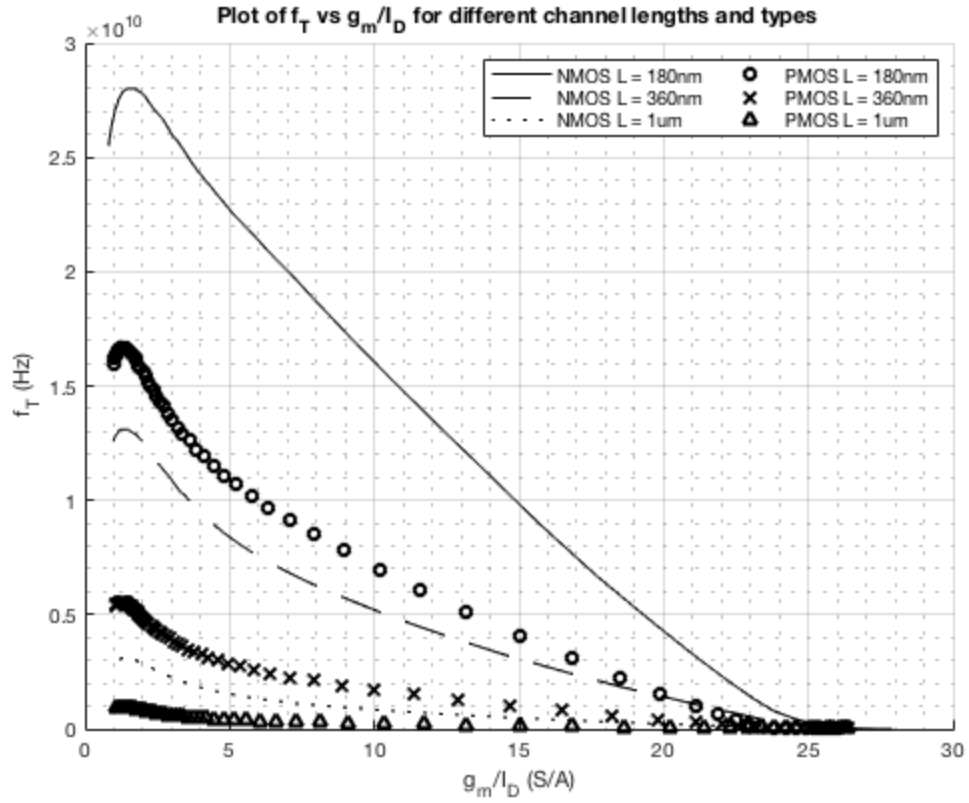

Published with MATLAB® R2018b

	Simulated gm/Id	Long Channel Estimate	% error
NMOS, L=0.18um, Vov=50mV	18.4079	40	-54%
NMOS, L=0.36um, Vov=50mV	19.5968	40	-51%
NMOS, L=0.36um, Vov=250mV	7.4286	8	-7%
NMOS, L=1um, Vov=250mV	7.8576	8	-2%
PMOS, L=0.18um, Vov=50mV	19.052	40	-52%
PMOS, L=0.36um, Vov=50mV	19.3004	40	-52%
PMOS, L=0.36um, Vov=250mV	7.6539	8	-4%
PMOS, L=1um, Vov=250mV	7.8037	8	-2%

As you can see, the long channel estimate is only appropriate for higher overdrive voltages (Vov).