

TP24222

pledged

Problem 1:

a) For proper current mirror operation, the transistors must be in saturation.

$$\text{So } V_{DS} \geq \overbrace{V_{GS} - V_T}^{V_{OV}}.$$

$$V_{in1} = V_{GS6} + V_{DS5} = V_{OV6} + V_T + V_{OV5}$$

$$V_{in1} = 2V_{OV} + V_T$$

$$V_{in2} = V_{OV} + V_T$$

$$b) \quad R_{out} = r_{o4}(1 + (g_{m4} + g_{mb4}) R_{d3}) + R_{d3} \quad R_{d3} = r_{o3}(1 + (g_{m3} + g_{mb3}) 0) \rightarrow 0$$

$$R_{out} = r_{o4}(1 + (g_{m4} + g_{mb4}) r_{o3}) + r_{o3}$$

$$R_{d3} = r_{o3}$$

$$R_{out} \approx (g_{m4} + g_{mb4}) r_{o3}^2$$

$$V_{OV, MIN} = 2V_{OV}$$

$$c) \quad R_{out} = \frac{1}{\lambda I_{out}} \Rightarrow \lambda = \frac{1}{R_{out} I_{out}}$$

$$V_{DS3} = V_{OV} \quad V_{DS1} = V_T$$

$$\epsilon = (V_{DS3} - V_{DS1}) \lambda = \frac{V_{OV} - V_T}{R_{out} I_{out}} = 0$$

$$V_{OV} = V_T$$

$$\text{or } V_{DS3} = V_{DS1}$$

d)

$$\lambda_{WSCCM} = \frac{\frac{g_{ds4}}{I_D}}{\frac{g_{m4}}{I_D} + \frac{g_{mb4}}{I_D} + \frac{g_{ds4}}{I_D} + 1} \lambda$$

$$\lambda = \frac{1}{I_D r_{o3}}$$

$$\lambda_{WSCCM} = \frac{1}{R_o I_D} = \frac{1}{(r_{o4}(1 + (g_{m4} + g_{mb4})r_{o3}) + r_{o3}) I_D}$$

$$= \frac{1}{(r_{o4}(1 + g_{m4}r_{o3} + g_{mb4}r_{o3}) + r_{o3}) I_D}$$

$$= \frac{1}{I_D r_{o4} + I_D r_{o4} g_{m4} r_{o3} + g_{mb4} r_{o3} I_D r_{o4} + r_{o3} I_D}$$


$$= \frac{1}{I_D} \frac{1}{r_{o4} + r_{o4} g_{m4} r_{o3} + g_{mb4} r_{o3} r_{o4} + r_{o3}}$$

$$= \frac{1}{I_D r_{o4}} \frac{1}{1 + g_{m4} r_{o3} + g_{mb4} r_{o3} + \frac{r_{o3}}{r_{o4}}}$$

$$= \frac{\frac{g_{ds4}}{I_D}}{\frac{1}{I_D r_{o3}} \left(1 + g_{m4} r_{o3} + g_{mb4} r_{o3} + \frac{r_{o3}}{r_{o4}} \right)} \frac{1}{I_D r_{o3}}$$

$$= \frac{\frac{g_{ds4}}{I_D}}{\frac{1}{I_D r_{o3}} + \frac{g_{m4}}{I_D} + \frac{g_{mb4}}{I_D} + \frac{1}{I_D r_{o4}}} \frac{1}{I_D r_{o3}}$$
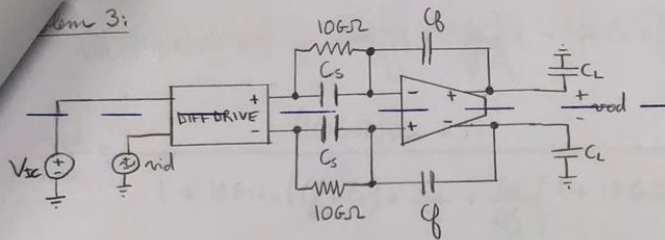
$$\lambda_{WSCCM} = \frac{\frac{g_{ds4}}{I_D}}{\frac{g_{m4}}{I_D} + \frac{g_{mb4}}{I_D} + \frac{g_{ds4}}{I_D} + 1} \lambda$$




$$C_s = 10 \text{ pF}$$

$$C_f = 10 \text{ pF}$$

$$C_L = 5 \text{ pF}$$

$$V_{ic} = 1.1 \text{ V}$$

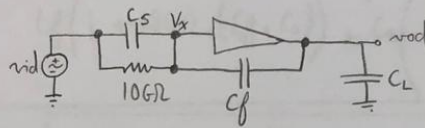

$$(v_{id} - v_x) s C_s + \frac{(v_{id} - v_x)}{10 \text{ G}\Omega} = (v_x - v_{out}) s C_f$$

$$v_{id} s C_s - v_x s C_s + \frac{v_{id}}{10 \text{ G}\Omega} - \frac{v_x}{10 \text{ G}\Omega} = v_x s C_f - v_{out} s C_f$$

$$v_x \left(s C_s + \frac{1}{10 \text{ G}\Omega} + s C_f \right) = v_{id} \left(s C_s + \frac{1}{10 \text{ G}\Omega} \right) + v_{out} s C_f$$

$$v_x = \frac{v_{id} \left(s C_s + \frac{1}{10 \text{ G}\Omega} \right) + v_{out} s C_f}{s C_s + \frac{1}{10 \text{ G}\Omega} + s C_f} = \frac{v_{id} (10 \text{ G}\Omega) s C_s + 1 + v_{out} s C_f (10 \text{ G}\Omega)}{(10 \text{ G}\Omega) (s C_s + s C_f) + 1}$$

$$(v_x - v_{out}) s C_f = v_{out} s C_s$$

$$v_x = v_{out} \left(1 + \frac{s C_s}{s C_f} \right)$$

$$\frac{v_{id} (10 \text{ G}\Omega) (s C_s + 1) + v_{out} s C_f (10 \text{ G}\Omega)}{(10 \text{ G}\Omega) (s C_s + s C_f) + 1} = v_{out} \left(1 + \frac{s C_s}{s C_f} \right)$$

$$v_{id}((10G\Omega)sC_s + 1) = v_{id}\left[\left(1 + \frac{C_s}{C_f}\right)(1 + 10G\Omega s(C_s + C_f)) - C_f(10G\Omega)\right]$$

$$\frac{v_{od}}{v_{id}} = \frac{(10G\Omega)sC_s + 1}{1 + 10G\Omega s(C_f + C_s) + \frac{C_s}{C_f} + \frac{C_s}{C_f}(1 + 10G\Omega s(C_s + C_f)) - sC_f(10G\Omega)}$$

$$\frac{v_{od}}{v_{id}} = \frac{C_f((10G\Omega)sC_s + 1)}{C_f(1 + 10G\Omega s(C_f + C_s)) + C_s\left(1 + (1 + 10G\Omega s(C_s + C_f))\right) - sC_f^2 10G\Omega}$$

$$\omega_{-3dB} = \frac{2C_s + C_f}{C_s^2(10G\Omega) + 20G\Omega(C_s C_f)}$$

$$\omega_{u} = \frac{2}{10G\Omega(C_s + C_f)} = \frac{1}{5G\Omega(C_s + C_f)}$$

$$v_{id}((10G\Omega)sC_s + 1) = v_{id}\left[\left(1 + \frac{C_s}{C_f}\right)(1 + 10G\Omega s(C_s + C_f)) - C_f(10G\Omega)\right]$$

$$\frac{v_{od}}{v_{id}} = \frac{(10G\Omega)sC_s + 1}{1 + 10G\Omega s(C_f + C_s) + \frac{C_s}{C_f} + \frac{C_s}{C_f}(1 + 10G\Omega s(C_s + C_f)) - sC_f(10G\Omega)}$$

$$\frac{v_{od}}{v_{id}} = \frac{C_f((10G\Omega)sC_s + 1)}{C_f(1 + 10G\Omega s(C_f + C_s)) + C_s\left(1 + (1 + 10G\Omega s(C_s + C_f))\right) - sC_f^2 10G\Omega}$$

$$\omega_{-3dB} = \frac{2C_s + C_f}{C_s^2(10G\Omega) + 20G\Omega(C_s C_f)}$$

$$\omega_{u} = \frac{2}{10G\Omega(C_s + C_f)} = \frac{1}{5G\Omega(C_s + C_f)}$$

em 4: Textbook Problem 8.28b) (Local shunt-shunt feedback amplifier).

$$R_f = 100 \text{ k}\Omega$$


$$R_L = 15 \text{ k}\Omega$$

$$I_D = 0.5 \text{ mA}$$


$$\frac{W}{L} = 100$$

$$k' = 180 \mu\text{A/V}^2$$

$$r_o = \infty$$

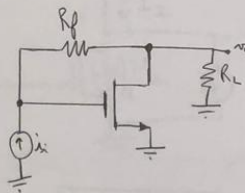

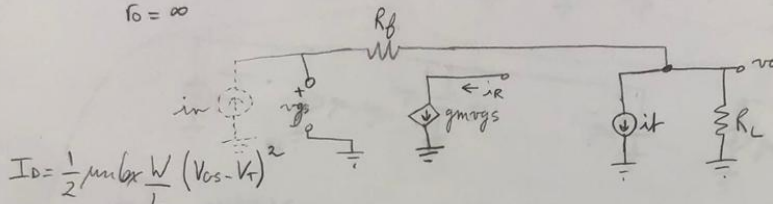Calculate: - loop gain.
- closed-loop gain.



$$I_D = \frac{1}{2} \mu_n k' \frac{W}{L} (V_{GS} - V_T)^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n k' \frac{W}{L} (V_{GS} - V_T) = k' \frac{W}{L} V_{OV} = \frac{2I_D}{V_{OV}}$$

$$V_{OV}^2 = \frac{2I_D}{k' \frac{W}{L}} \Rightarrow V_{OV} = \sqrt{\frac{2I_D}{k' \frac{W}{L}}} = 0.2357 \text{ V}$$

$$g_m = \frac{2I_D}{V_{OV}} = 4.243 \text{ mS}$$

$$i_t = \frac{0 - v_o}{R_L} = -\frac{v_o}{R_L}$$

$$i_R = g_m v_{gs} = g_m v_o$$

$$T = -\frac{i_R}{i_t} = -\frac{g_m v_o}{-\frac{v_o}{R_L}} = g_m R_L$$

$$\Rightarrow \text{Loop gain} = T = g_m R_L = 63.645$$

$$A = A_{\infty} \frac{T}{T+1} + \frac{d}{T+1}$$


$$\text{Closed loop gain} = A_{\infty} = -R_f = -100 \text{ k}\Omega$$

$$A_{\infty} = \left. \frac{v_o}{i_{in}} \right|_{g_m = \infty} = -R_f$$

$$\text{when } g_m = \infty \Rightarrow v_{gs} = 0$$

$$i_{in} = \frac{0 - v_o}{R_f} \Rightarrow \frac{v_o}{i_{in}} = -R_f$$



Problem 5: v_1, I_1

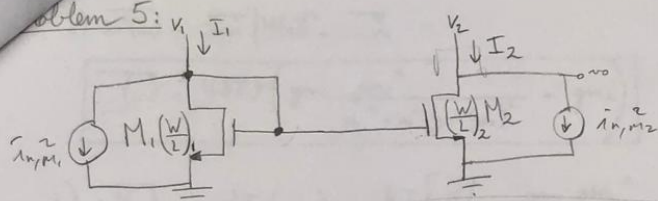

$$L_1 = L_2$$


$$W_2 = M \cdot W_1$$

$$\gamma_1 = \gamma_2 = \gamma$$

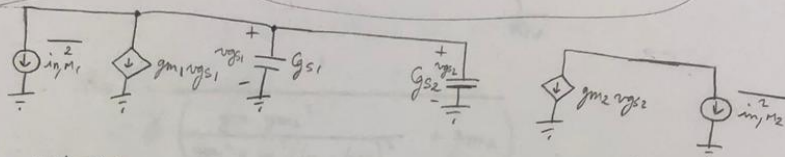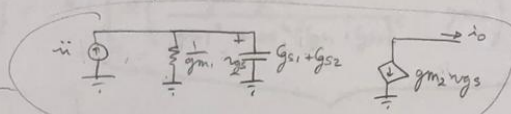

$$\overline{i_{n,M1}^2} = 4kT\gamma gm_1$$
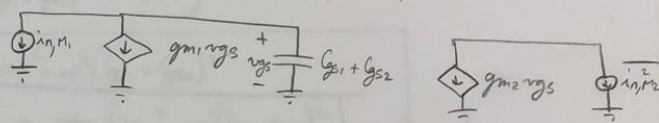
$$\overline{i_{n,M2}^2} = 4kT\gamma gm_2$$



$$i_0 = -gm_2 v_{gs} = -gm_2 i_i \left(\frac{1}{gm_1} \parallel \frac{1}{s(g_{s1} + g_{s2})} \right)$$

$$H(s) = \frac{i_0(s)}{i_i(s)} = -gm_2 \left(\frac{1}{gm_1} \parallel \frac{1}{s(g_{s1} + g_{s2})} \right)$$

$$H(s) = -gm_2 \frac{\frac{1}{gm_1 s(g_{s1} + g_{s2})}}{\frac{1}{gm_1} + \frac{1}{s(g_{s1} + g_{s2})}} = \frac{-gm_2}{gm_1 + s(g_{s1} + g_{s2})}$$

$$|H(s)| = \frac{gm_2}{\sqrt{gm_1^2 + \omega^2(g_{s1} + g_{s2})^2}}$$

$$|H(s)|^2 = \frac{gm_2^2}{gm_1^2 + \omega^2(g_{s1} + g_{s2})^2}$$

$$a) \overline{i_0^2(\omega)} = \overline{i_{n,M1}^2} |H(s)|^2 + \overline{i_{n,M2}^2}$$

$$a) \overline{i_o^2(\omega)} = \overline{i_{n,M1}^2} |H(s)|^2 + \overline{i_{n,M2}^2}$$

$$\overline{i_o^2(\omega)} = 4kT\gamma \left(\frac{g_{m1} g_{m2}^2}{g_{m1}^2 + \omega^2 (g_{s1} + g_{s2})^2} + g_{m2} \right)$$


$$b) \overline{i_o^2(\omega)} = 4kT \left(\frac{1}{R_N} \right) = 4kT \underbrace{\left[\gamma \left(\frac{g_{m1} g_{m2}^2}{g_{m1}^2 + \omega^2 (g_{s1} + g_{s2})^2} + g_{m2} \right) \right]}_{\frac{1}{R_N}}$$

$$R_N = \frac{1}{\gamma \left(\frac{g_{m1} g_{m2}^2}{g_{m1}^2 + \omega^2 (g_{s1} + g_{s2})^2} + g_{m2} \right)}$$

$$R_N = \frac{1}{\gamma} \frac{g_{m1}^2 + \omega^2 (g_{s1} + g_{s2})^2}{g_{m1} g_{m2}^2 + g_{m2} (g_{m1}^2 + \omega^2 (g_{s1} + g_{s2})^2)}$$

- To minimize the noise, you want to maximize R_N .
- Maximizing R_N entails maximizing g_{m1} and minimizing g_{m2} .
- So you want to minimize M , since $M \propto \frac{g_{m2}}{g_{m1}}$

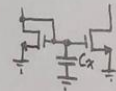c) To minimize the overall output noise contribution of the current mirror, attach a large capacitor (C_x) between the gate voltage and ground \Rightarrow



$$R_{N\text{resulting}} = \frac{1}{\gamma} \frac{g_{m1}^2 + \omega^2 (g_{s1} + g_{s2} + C_x)^2}{g_{m1} g_{m2}^2 + g_{m2} (g_{m1}^2 + \omega^2 (g_{s1} + g_{s2} + C_x)^2)}$$

$$\text{Assume } C_x \gg g_{s1} + g_{s2} \Rightarrow R_{N\text{resulting}} \approx \frac{1}{\gamma} \frac{\omega^2 C_x^2}{g_{m2} \omega^2 C_x^2} \approx \frac{1}{\gamma g_{m2}}$$

d) The noise of this mirror would be much greater than that of a resistor that provides the same output resistance as the mirror. Ho


$$\Rightarrow \overline{i_{n, \text{mirror}}^2} = \frac{4kT}{R_N}$$

$$\overline{i_{n, R_o}^2} = \frac{4kT}{r_o}$$

$$R_N \ll r_o, \text{ so } \overline{i_{n, R_o}^2} \ll \overline{i_{n, \text{mirror}}^2}$$

However, replacing the mirror with such a resistor would completely annihilate the headroom at the output of the circuit, since the value of r_o is usually on the order of hundreds of $k\Omega$. So the voltage drop across r_o would probably be the same as the supplied voltage.

Problem 6:

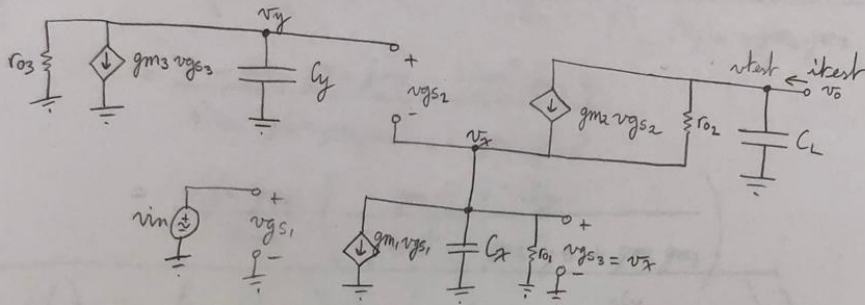

a)
$$v_x = \left(-g_{m1} v_{in} + g_{m2} (v_y - v_x) \right) \frac{1}{sL_x} \quad v_0 = -g_{m2} (v_y - v_x) \frac{1}{sC_L}$$

$$v_x = \left(-g_{m1} v_{in} + g_{m2} \left(-\frac{g_{m3} v_x}{sL_y} - v_x \right) \right) \frac{1}{sL_x} \quad v_0 = -g_{m2} \left(-\frac{g_{m3} v_x}{sL_y} - v_x \right) \frac{1}{sC_L}$$

$$\frac{v_x}{v_{in}} = \frac{-g_{m1} sL_y}{sL_y sL_x + g_{m2} (g_{m3} + sL_y)}$$

$$v_y = -g_{m3} v_x \frac{1}{sL_y}$$

$$\frac{v_y}{v_x} = \frac{-g_{m3}}{sL_y}$$

$$v_0 = \frac{-g_{m2}}{sC_L} v_x \left(\frac{-g_{m3}}{sL_y} - 1 \right)$$

$$\rightarrow H(s) = \frac{v_0}{v_{in}} = \frac{v_0}{v_x} \frac{v_x}{v_{in}} = \frac{g_{m2}}{sC_L} \left(\frac{g_{m3}}{sL_y} + 1 \right) \frac{-g_{m1} sL_y}{s^2 L_y L_x + g_{m2} (g_{m3} + sL_y)}$$

$$= \left(\frac{g_{m2} g_{m3}}{C_L L_y s^2} + \frac{g_{m2}}{sC_L} \right) \frac{-g_{m1} sL_y}{s^2 L_y L_x + g_{m2} g_{m3} + g_{m2} sL_y}$$

$$= \frac{g_{m2}}{sC_L} \left(\frac{g_{m3}}{sL_y} + 1 \right) \frac{-g_{m1} sL_y}{s^2 L_y L_x + g_{m2} g_{m3} + g_{m2} sL_y}$$

$$= -\frac{g_{m1} g_{m2} L_y}{C_L} \left(\frac{g_{m3}}{sL_y} + 1 \right) \frac{1}{s^2 L_y L_x + g_{m2} g_{m3} + g_{m2} sL_y}$$

$$H(s) = \left(\frac{-g_{m1} g_{m2} g_{m3}}{s C_L} - \frac{s g_{m1} g_{m2} C_y}{s C_L} \right) \left(\frac{1}{s^2 C_y C_x + g_{m2} g_{m3} + g_{m2} s C_y} \right)$$

$$= \frac{-g_{m1} g_{m2} g_{m3} - s g_{m1} g_{m2} C_y}{s^3 C_L C_y C_x + g_{m2} g_{m3} C_L s + g_{m2} C_y C_L s^2}$$

$$= \frac{-g_{m1} g_{m2}}{s C_L} \left(\frac{g_{m3} + s C_y}{C_y C_x s^2 + g_{m2} C_y s + g_{m2} g_{m3}} \right)$$

$$H(s) = \underbrace{-g_{m1} g_{m2} g_{m3}}_{\text{DC gain}} \underbrace{\frac{1}{s C_L} \left(\frac{1 + \frac{s C_y}{g_{m3}}}{C_y C_x s^2 + g_{m2} C_y s + g_{m2} g_{m3}} \right)}_{\text{Freq. Dependence}}$$

DC gain

Freq. Dependence


$$H(s) = -g_{m1} \frac{1}{s C_L} \left(\frac{1 + \frac{s C_y}{g_{m3}}}{\frac{C_y C_x}{g_{m2} g_{m3}} s^2 + \frac{C_y}{g_{m3}} s + 1} \right)$$

Dominant pole $\frac{-g_{m1}}{s C_L} = 1$

Assume the 2 other poles
and the zero appear far after the dominant
pole.

$$W_u = \frac{g_{m1}}{C_L}$$

From sect 3.4.3:

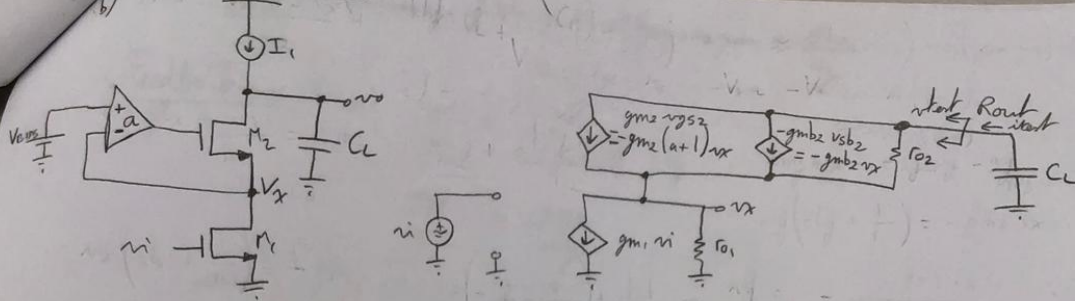

$$V_{gs2} = V_{g2} - V_{s2} = -a v_x - v_x = -v_x(1+a)$$

$$i_{test} = \frac{v_{test} - v_x}{r_{o2}} - g_{m2}(a+1)v_x - g_{mb2}v_x$$

$$i_{test} = \frac{v_x}{r_{o1}}$$

$$\frac{v_x}{r_{o1}} = \frac{v_{test}}{r_{o2}} - \frac{v_x}{r_{o2}} - g_{m2}(a+1)v_x - g_{mb2}v_x$$

$$v_x \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{mb2} + g_{m2}(a+1) \right) = \frac{v_{test}}{r_{o2}}$$

$$v_x = \frac{1}{r_{o2} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{mb2} + g_{m2}(a+1) \right)} v_{test}$$

$$i_{test} = \frac{v_x}{r_{o1}} = \frac{1}{r_{o1} r_{o2} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{mb2} + g_{m2}(a+1) \right)} v_{test}$$

$$\frac{v_{test}}{i_{test}} = R_{out} = r_{o2} + r_{o1} + r_{o1} r_{o2} (g_{mb2} + g_{m2}(a+1))$$

$$R_{out} \approx r_{o1} r_{o2} (g_{mb2} + g_{m2}(a+1))$$

$$Z_{out} = R_{out} \parallel \frac{1}{sC_L}$$

c) Unity gain frequency of the feedback loop is $\omega_u = \frac{g_{m3}}{C_y}$

Feedback circuit $\Rightarrow \frac{v_y}{v_x} = - \frac{g_{m3}}{1 + g_{m3}(0)} \frac{1}{s C_y}$

$$\frac{v_y}{v_x} = - \frac{g_{m3}}{s C_y}$$

$$\frac{v_x}{v_y} = \frac{g_{m2} \frac{1}{s C_x}}{1 + g_{m2} \frac{1}{s C_x}} = \frac{1}{1 + \frac{s C_x}{g_{m2}}}$$

Unity gain frequency = $\frac{g_{m3}}{C_y}$

From $\frac{v_x}{v_y}$ expression, second pole activates at $\frac{g_{m2}}{C_x}$.

So to have 45° phase margin, 2nd pole must kick in after ω_u .

$$\boxed{\frac{g_{m2}}{C_x} \geq \frac{g_{m3}}{C_y}}$$